SCIENCE

Class 10 | Practice set | 2026

Time allowed: 60 minutes | Maximum marks: 25

General instructions

Attempt all six questions. Marks for each question are shown in brackets.

Show working and give examples where relevant.

This short sample is not an official CBSE or school examination paper.

SECTION A - CONCEPTS & APPLICATION

1. State Ohm’s law. Write the SI units of potential difference and resistance. **[3]**

2. Why are household appliances connected in parallel? Give two reasons. **[4]**

3. Calculate the current through a 12 Ω resistor connected to a 6 V battery. **[4]**

SCIENCE

Class 10 | Practice set | 2026

Time allowed: 60 minutes | Maximum marks: 25

SECTION B - EXTENDED PRACTICE

4. A wire of resistance R is stretched to twice its length. How does its resistance change? **[4]**

5. Derive the expression for the equivalent resistance of two resistors in series. **[5]**

6. An electric heater draws 5 A from a 220 V supply. Calculate the energy consumed in 30 minutes. **[5]**